



STAMFORD COLLEGE

SCHOOL OF ENGINEERING

FOUNDATION STUDIES IN ENGINEERING (ELECTRICAL AND ELECTRONIC)

KE009: Electric Circuits

Date : 6th Sep 2007 (Thursday)

Time : 10.00 am – 12.00 am

Duration: 2 hours + 10 minutes reading time

Instructions to Candidates

1. SIX questions set.
2. Answer any FOUR questions.
3. All questions carry equal marks.
4. Maximum marks attainable: 100

Please ensure that this examination paper contains SIX questions on SIX printed pages before you start the examination.

Books, papers and other written materials are not allowed to be brought into the examination hall. A candidate who violates the examination rules of Stamford College or commits a malpractice will be disqualified from the examination.

Write your Examination Index Number on each page of your answer booklet.

Answer any FOUR questions.

Question 1

a) Define the following terms:

- i) Current
- ii) Power

(4 marks)

b) Calculate the amount of electrons passing through a fixed point in a 100 W bulb in one hour if the applied voltage is 120 V.

(6 marks)

c) The resistance of a 200 m long copper wire is 21Ω and its thickness is 0.44 mm. Calculate its specific resistance.

(5 marks)

d) A potentiometer of resistance 80Ω is connected across a supply of 120 V as shown in Figure Q1(a). A current of 2 A is required in the 10Ω resistor.

- i) Calculate the resistance between points A and B
- ii) Find the position of the tapping point C.

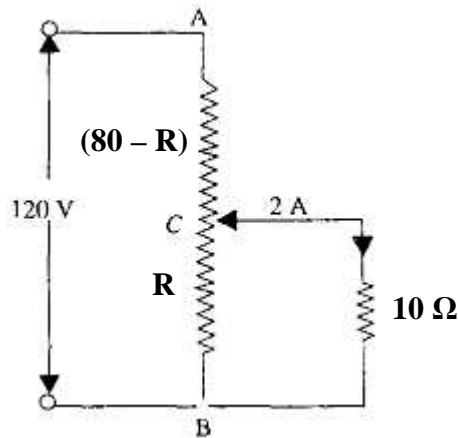


Figure Q1(a)

(10 marks)
(Total = 25 marks)

Question 2

a) State Ohm's Law.

(2 marks)

b) Three resistors of $2\ \Omega$, $1\ \Omega$ and $5\ \Omega$ are connected in series with a $20\ \text{V}$ supply as shown in Figure Q2(b). Calculate:

- i) the total resistance
- ii) the total current
- iii) the potential difference across each resistor
- iv) the power

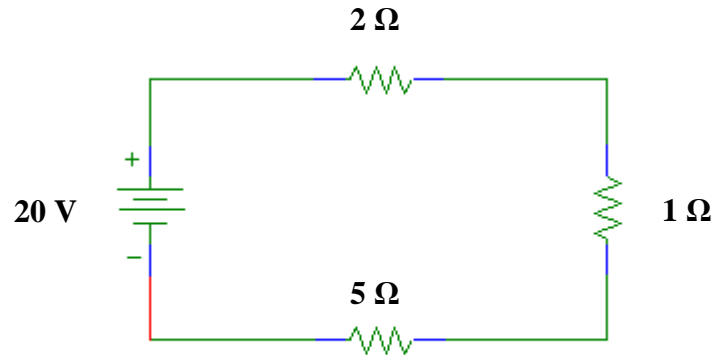


Figure Q2(b)

(7 marks)

c) For the parallel circuit shown in Figure Q2(c), calculate:

- i) the equivalent resistance
- ii) the current in each branches
- iii) the total current

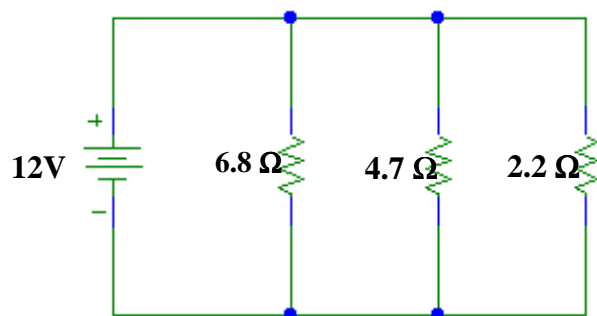


Figure Q2(c)

(10 marks)

- e) For the circuit shown in Figure Q2 (d), calculate the total power (P) supplied by the 12 V battery.

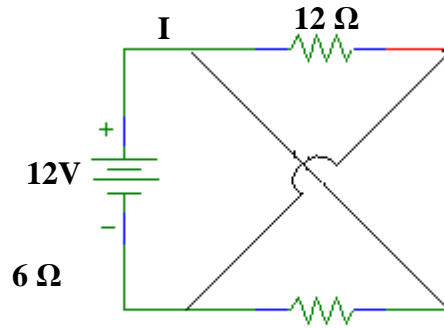


Figure Q2(d)

(6 marks)
(Total = 25 marks)

Question 3

- a) State Kirchhoff's Voltage Law and Kirchhoff's Current Law. (5 marks)
- b) A wheatstone bridge network is shown in Figure Q3(b): Resistances between AB, BC, CD, DA and BD are 40,20,10,20 and 30 Ω respectively. A 2 V battery of negligible internal resistance is connected between A and C. Determine the current flowing through the 50 Ω resistor.

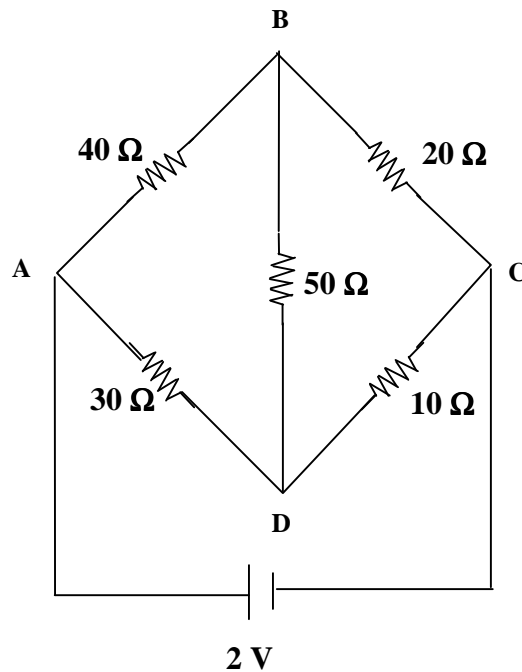


Figure Q3 (b)

(10 marks)

- c) Formulate the Kirchhoff's voltage law equation for the circuit shown in Figure Q3(c) and determine the current flowing through the 132 Ω resistor.

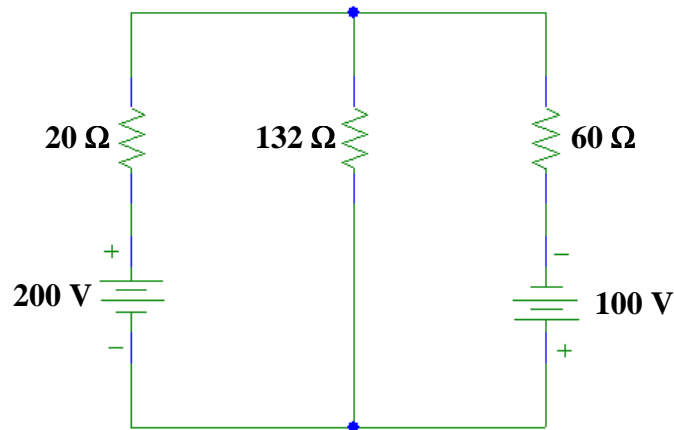


Figure Q3(c)

(10 marks)
(Total= 25 marks)

Question 4

- a) A coil of 100 turns has an inductance of 0.15 H. Calculate :
- i) the total magnetic flux through the coil when the current is 4 A
 - ii) the energy stored in the magnetic field
 - iii) the voltage induced in the coil when the current is reduced to zero in 0.01 second.
- (6 marks)
- b) Find the equivalent inductance for the circuit of Figure Q 4(a)

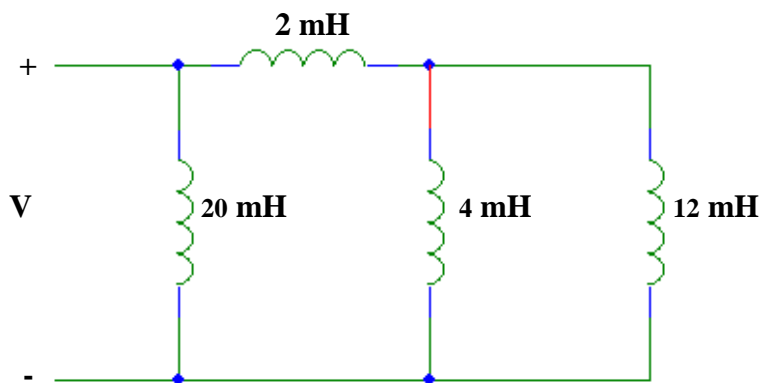


Figure Q4 (a)

(5 marks)

- c) A capacitor of capacitance $4 \mu\text{F}$ is fully charged from a 12 V d.c. supply. Calculate:
- the charge stored by the capacitor
 - the energy delivered by the supply
 - the energy stored by the capacitor
- (6 marks)
- d) A $2 \mu\text{F}$, $3 \mu\text{F}$ and $6 \mu\text{F}$ capacitors are connected in series to a 500 V source. Calculate:
- the equivalent capacitance
 - the charge across each capacitor
 - the potential difference across each capacitor
- (8 marks)
(Total=25 marks)

Question 5

- a) Define the following:
- root mean square(r.m.s) value
 - Form Factor
- (4 marks)
- b) An e.m.f given by the expression $v(t) = 200 \sin \omega t$ is applied to a 25Ω resistor. Determine:
- the instantaneous current
 - the instantaneous power
 - the average power
- (6 marks)
- c) A sinusoidal alternating voltage of 50 Hz has an r.m.s value of 200 V .
- Write an equation for instantaneous value of voltage.
 - Draw the waveform and mark the values.
- (5 marks)
- d) A $200 \mu\text{F}$ capacitor is connected to a $200 \text{ V}, 50 \text{ Hz}$ supply.
- Calculate the capacitive reactance.
 - Write an equation for instantaneous value of voltage
 - Calculate the r.m.s value of current
 - Calculate the instantaneous power
 - Determine the average power.
- (10 marks)
(Total= 25 marks)

Question 6

a) A coil of resistance of $10\ \Omega$ and an inductance of $0.1\ \text{H}$ is connected in series with a capacitor of $150\ \mu\text{F}$ across a $200\ \text{V}, 50\ \text{Hz}$ supply. Calculate:

- i) the impedance
- ii) the current
- iii) the power factor
- iv) the voltage across the coil and
- v) the voltage across the capacitor

(10 marks)

b) An a.c series circuit has a resistance of $10\ \Omega$, an inductance of $0.2\ \text{H}$ and a capacitance of $60\ \mu\text{F}$. If the applied input voltage is $200\ \text{V}$, calculate:

- i) the resonant frequency
- ii) the current and
- iii) the power at resonance

(7 marks)

c) Compare series and parallel resonance circuits.

(8 marks)

(Total = 25 marks)

– END OF PAPER –